

2020-1 컴퓨터 조직론

# Project 1. Getting Started

Juhee Kim

System & software security Lab.

Seoul National University

Apr. 10, 2020

# Table of Contents

- Project Goals
- Contents
  - Step 1: Getting Started with Chisel
  - Step 2: Create your First Chisel Hardware
  - Step 3: Simulating and testing the circuit
- Evaluation Criteria
- Submission

# Project Goals

- Learn how to use Chisel
- Learn how to run tests and debug Chisel
- Make your first hardware with Chisel

# Step 1: Getting Started with Chisel

- Chisel Overview

- **Chisel** is a hardware design language that facilitates **advanced circuit generation and design reuse for both ASIC and FPGA digital logic designs.**

- Chisel References

- Chisel Homepage  
<https://www.chisel-lang.org/>
- Chisel Wiki  
<https://github.com/freechipsproject/chisel3/wiki>

# Step 1: Getting Started with Chisel

- Datatypes in Chisel

```
Bool()          // Bool literals (1-bit)
  true.B
  false.B

UInt()          // unsigned int, width inferred
UInt(32.W)      // 32-bit unsigned decimal
  1.U           // unsigned decimal 1-bit literal
  5.U           // unsigned decimal 3-bit literal
  8.U(4.W)      // 4-bit unsigned decimal, value 8
  "b001010".U  // 6-bit binary literal

SInt()          // signed int, width inferred
  5.S           // signed 4-bit literal
  -8.S          // signed negative 4-bit literal
```

***You may get an error if  
it can't infer the width***

```
// variable declaration
```

```
val b = true.B
val sint = 3.S(4, W)
```

# Step 1: Getting Started with Chisel

- Wires

- **Create** a new wire


*use '=' operator to create a new variable*

```
val x = Wire(UInt())
```

- **Connect** two wires

```
y := x
```
 
```
val adder1 = Module(new Adder())  
val adder2 = Module(new Adder())  
  
adder2.io.inputx := adder1.io.result
```



# Step 1: Getting Started with Chisel

- Getting parts of a wire

```
val x = Wire(UInt(32.W))
val lower_5 = x(4,0)
val top_3 = x(31,29)
val rd_in_riscv_instruction = x(11,7)
```

- Built-in Operators →

- Equality is '==='.

## Operators:


Chisel	Explanation	Width
!x	Logical NOT	1
x && y	Logical AND	1
x    y	Logical OR	1
x(n)	Extract bit, 0 is LSB	1
x(n, m)	Extract bitfield	n - m + 1
x << y	Dynamic left shift	w(x) + maxVal(y)
x >> y	Dynamic right shift	w(x) - minVal(y)
x << n	Static left shift	w(x) + n
x >> n	Static right shift	w(x) - n
Fill(n, x)	Replicate x, n times	n * w(x)
Cat(x, y)	Concatenate bits	w(x) + w(y)
Mux(c, x, y)	If c, then x; else y	max(w(x), w(y))
~x	Bitwise NOT	w(x)
x & y	Bitwise AND	max(w(x), w(y))
x   y	Bitwise OR	max(w(x), w(y))
x ^ y	Bitwise XOR	max(w(x), w(y))
x === y	Equality (triple equals)	1
x != y	Inequality	1
x != y	Inequality	1
x + y	Addition	max(w(x), w(y))
x +% y	Addition	max(w(x), w(y))
x +& y	Addition	max(w(x), w(y)) + 1
x - y	Subtraction	max(w(x), w(y))
x -% y	Subtraction	max(w(x), w(y))
x -& y	Subtraction	max(w(x), w(y)) + 1
x * y	Multiplication	w(x) + w(y)
x / y	Division	w(x)
x % y	Modulus	bits(maxVal(y) - 1)
x > y	Greater than	1
x >= y	Greater than or equal	1
x < y	Less than	1
x <= y	Less than or equal	1
x >> y	Arithmetic right shift	w(x) - minVal(y)
x >> n	Arithmetic right shift	w(x) - n

# Step 1: Getting Started with Chisel

- Muxes

```
val x = Wire(UInt())  
x := Mux(selector, true_val, false_val)
```
 
```
val x = Wire(UInt(3.W))  
  
when(value === 0.U) {  
  x := "b001".U  
} .elsewhen (value > 0.S) {  
  x := "b010".U  
} .otherwise { // value must be <0  
  x := "b100.U"  
}
```



*Don't forget '.' in front of  
'elsewhen' and 'otherwise'.*



# Step 1: Getting Started with Chisel

- Muxes
  - switch-is statement for logic table

*You cannot have a "nested" switch-is statement. (use Mux or when statements instead.)*

input	output
0001	true
0100	false
0101	true
1101	true

```
// since we aren't fully specifying the
// output, Dontcare is required.
```

```
output := DontCare
```

```
switch(input) {
  is ("b0001".U) { output := true }
  is ("b0100".U) { output := false }
  is ("b0101".U) { output := true }
  is ("b1101".U) { output := true }
}
```


# Step 1: Getting Started with Chisel

- State elements (Registers)

```
val register = Reg(UInt(32.W))  
x := register  
register := y
```

*This will set the register to the value to on wire y at the end of the clock cycle*
 
```
// initializing register  
val register = RegInit(false.B)
```



# Step 1: Getting Started with Chisel

- Bundles

- group a set of wires together. (similar with struct in C)

```
class Complex extends Bundle {
  val real = SInt(32.W)
  val imag = SInt(32.W)
}
```

```
val wire = Wire(new Complex())           // create a wire with Complex type
val myreg = Reg(new Complex())           // create a register with Complex type

wire.real := 3.S                         // set each component of the wire
wire.imag := -5.S                       // or, set the entire bundle to 0
wire := 0.U.asTypeOf(new Complex)       // using an explicit cast

wire := myreg                           // connect the entire bundle of wires to
// other objects.
```

# Step 1: Getting Started with Chisel

- Modules

```
class Mux2 extends Module {  
  val io = IO (new Bundle {  
    val sel = Input(UInt(1.W))  
    val in0 = Input(UInt(1.W))  
    val in1 = Input(UInt(1.W))  
    val out = Output(UInt(1.W))  
  })  
  io.out := (io.sel & io.in1) | (~io.sel & io.in0)  
}
```

```
class Mux4 extends Module {  
  val io = IO(new Bundle {  
    val in0 = Input(UInt(1.W))  
    val in1 = Input(UInt(1.W))  
    val in2 = Input(UInt(1.W))  
    val in3 = Input(UInt(1.W))  
    val sel = Input(UInt(2.W))  
    val out = Output(UInt(1.W))  
  })  
  val m0 = Module(new Mux2)  
  m0.io.sel := io.sel(0)  
  m0.io.in0 := io.in0  
  m0.io.in1 := io.in1  
  
  val m1 = Module(new Mux2)  
  m1.io.sel := io.sel(1)  
  m1.io.in0 := io.in2  
  m1.io.in1 := io.in3  
  
  val m3 = Module(new Mux2)  
  m3.io.sel := io.sel(1)  
  m3.io.in0 := m0.io.out  
  m3.io.in1 := m1.io.out  
  
  io.out := m3.io.out  
}
```

## Step 2: Create your First Chisel Hardware

- Download the project file from [http://compsec.snu.ac.kr:40404/downloads/proj1\\_hw.tar.gz](http://compsec.snu.ac.kr:40404/downloads/proj1_hw.tar.gz)
- SimpleSystem Preparation
  - Create a new file (from the base directory)

```
touch src/main/scala/simple.scala
```

- Import the chisel libraries. Add the following lines to the `src/main/scala/simple.scala`

```
package dinocpu  
import chisel3._  
import chisel3.util._
```

# Step 2: Create your First Chisel Hardware

- System configuration

- Module SimpleAdder

- Input

- inputx: 32bit unsigned
      - inputy: 32bit unsigned

- Output

- result: 32bit unsigned

- Module SimpleSystem


- Goal: described in the figure.

- Output

- success: bool

- Variables

- adder1, adder2: SimpleAdder Modules

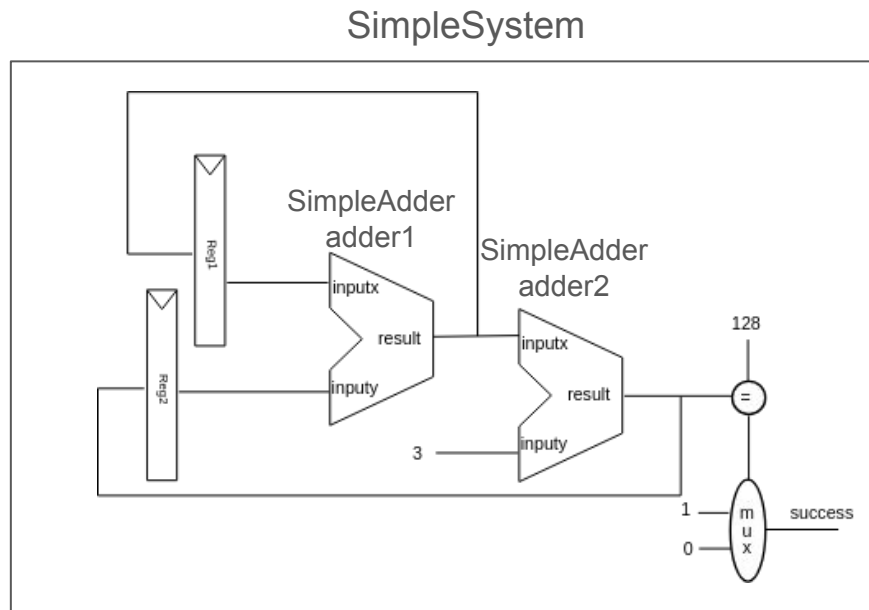

## Step 3: Simulating and testing the circuit

- Run singularity and test the circuit
  - Run singularity

```
singularity run library://jlowepower/default/dinocpu
```

You should see the following:

```
...  
[info] Loading settings for project root from build.sbt ...  
[info] Set current project to dinocpu (in build file:...)  
[info] sbt server started at ...  
sbt:dinocpu>
```

## Step 3: Simulating and testing the circuit

- Run singularity and test the circuit
  - Run test

```
sbt:dinocpu> test
```

```
[info] Compiling 1 Scalar source to ...  
...  
test SimpleSystem Success: 0 tests passed in 15 cycles taking  
0.016592 seconds  
[info] [0.007] RAN 10 CYCLES PASSED  
...  
[info] All tests passed
```

You can add `printf` to `SimpleSystem` to see what's going on inside it.

```
printf(p"reg1: $reg1, reg2: $reg2, success: ${io.success}\n")
```



# Evaluation Criteria

- Results for 10 cycles should be same with below.

```
reg1: 1, reg2: 4, success: 0
reg1: 5, reg2: 8, success: 0
reg1: 13, reg2: 16, success: 0
reg1: 29, reg2: 32, success: 0
reg1: 61, reg2: 64, success: 1
reg1: 125, reg2: 128, success: 0
reg1: 253, reg2: 256, success: 0
reg1: 509, reg2: 512, success: 0
reg1: 1021, reg2: 1024, success: 0
reg1: 2045, reg2: 2048, success: 0
```

# Submission

- Deadline: 2020. 04. 17 금요일 23:59
- 제출 방법: 서버에 본인이 구현한 **src 디렉토리를 그대로 복사해서 업로드**
  - 제출 서버: 147.46.114.111 (port 40404) ID: arch-<학번> / PW: dinocpu
  - 서버 패스워드 바꾸기
  - `$ ssh arch-<학번>@147.46.114.111 -p 40404`
  - `$ passwd`